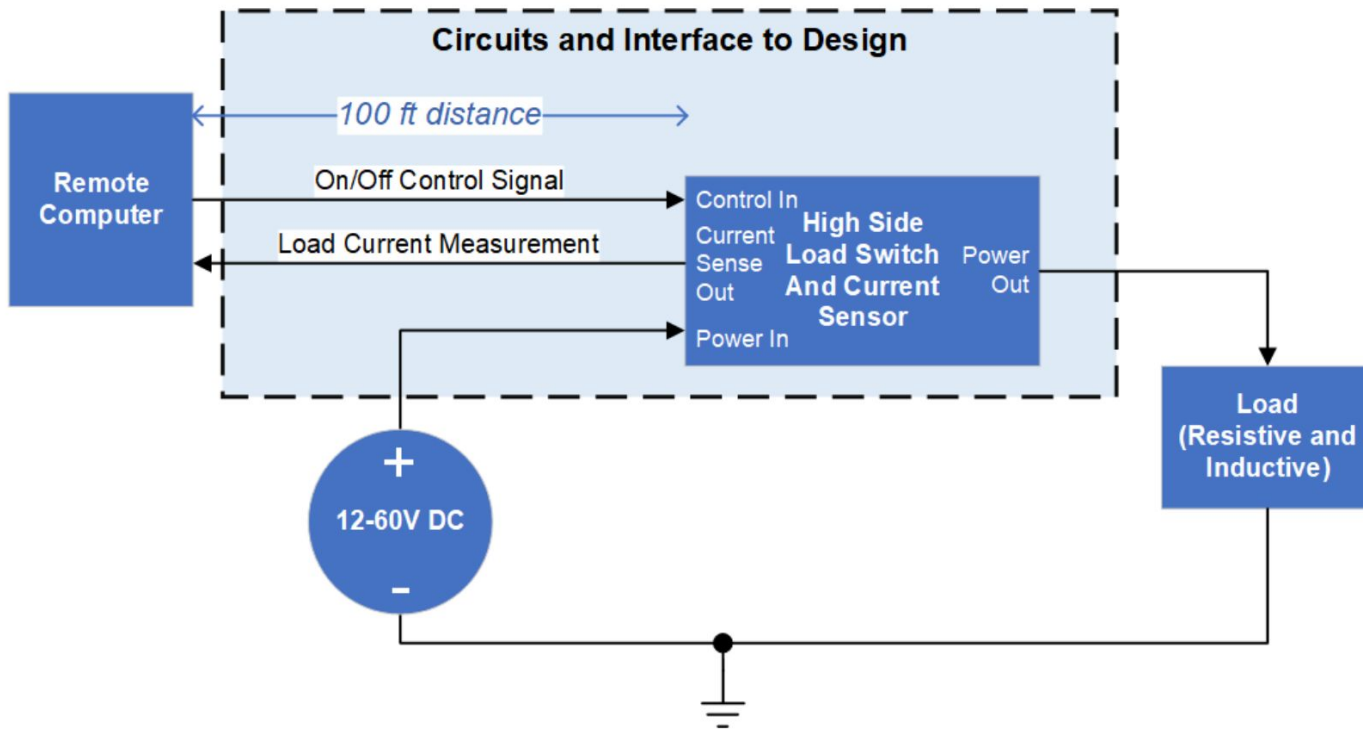


# Design Challenge: Remote Load Switch



# Power Requirements

Parameter	Value			Units	Note
	Min	Typ	Max		
$V_{\text{supply}}$	12		60	VDC	Voltage of supply to be switched.
$I_{\text{load}}$			10	A	Current into load.
$L_{\text{load}}$			5	mH	Load inductance.
$f_{\text{switch}}$			1	Hz	Continuous switching frequency.

- Probably want to switch high-side with a PMOS so load is at 0V when OFF.
- Inductive load needs flywheel diode for protection. No optimizations required for fast turn-off.
- Should oversize  $V_{\text{ds}}$  and  $I_{\text{ds}}$  of switching MOSFET to be safe.
- Gate drive requirements are pretty loose (not doing high frequency switching).

# Environmental Requirements

Parameter	Value			Units	Note
	Min	Typ	Max		
$T_{\text{ambient}}$	-40		70	°C	Ambient temperature.
$p_{\text{atm}}$	100		10	kPa	Atmospheric pressure.
EMI			Some		Conducted / radiated EMI.
Shock / Vibe			Moderate		Mechanical shock and vibration.

- Most industrial / commercial / automotive components meet the temperature spec.
- Don't need to qualify for vacuum, but maybe add pressure relief to enclosures?
- Add filters to power supply for reduced EMI in and out.
- Use differential signals, galvanically isolate comms to reduce ground loops.
- Need to be careful with component mass and dimensions, may need potting or celastic on big / dangly stuff, lots of PCB mounting points. Test for vibe modes.

# Measurement and Communication Requirements


Parameter	Value			Units	Note
	Min	Typ	Max		
$d_{\text{comms}}$			100	ft	Communication link distance.
$e_{\text{current}}$	-10		10	mA	Current measurement error.
$f_{\text{data}}$	100			Hz	Data sample and reporting rate.

- Long data link distance, probably need differential signals with decent transceivers. Digitize analog signals for lower noise and simpler combined interface.
- Need pretty high resolution and accuracy for current measurement. Need to pay attention to component tolerances and ADC resolution. Dynamic range is ~1:1000 (12-bit ADC only has 4096 counts, and the last few bits aren't usable).
- Data reporting rate is rather low, could probably get away with UART -> RS-485.


# Additional Thoughts

- Power switch needs to be fail-safe and difficult to damage.
  - Reverse polarity protection, undervoltage protection, overcurrent protection.
  - Need overcurrent protection to be fast-acting for short-circuits but compatible with capacitive loads.
  - Unprotected failure modes should result in the switch failing open (load is OFF).
- Switch should self-recover from faults.
- Switch should be able to report fault conditions when / after they occur.
- Switch should be able to report bus voltage.


# Simplified Block Diagram

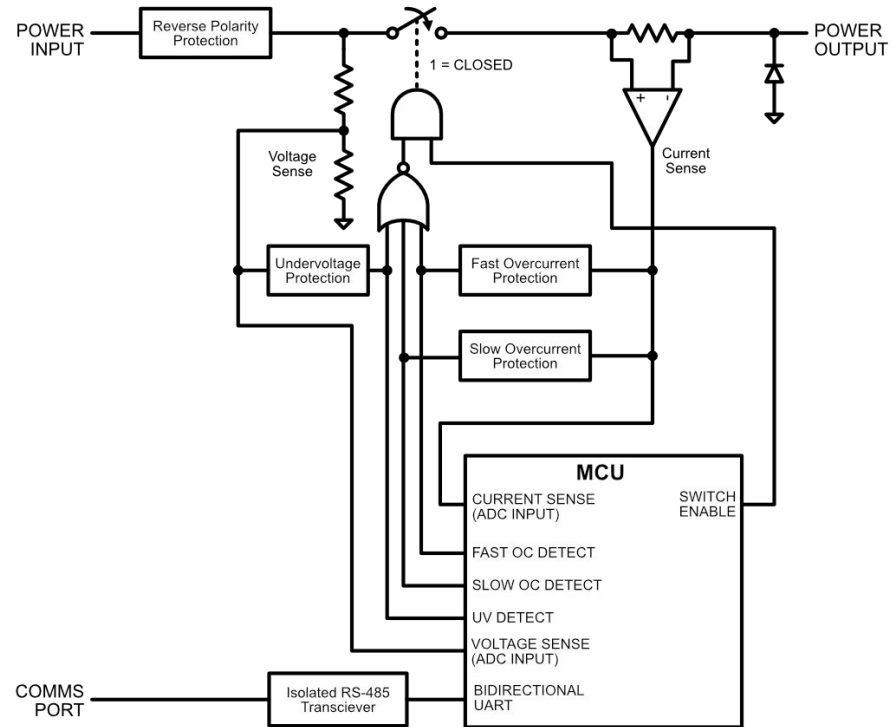

# Simplified Block Diagram: Power Input

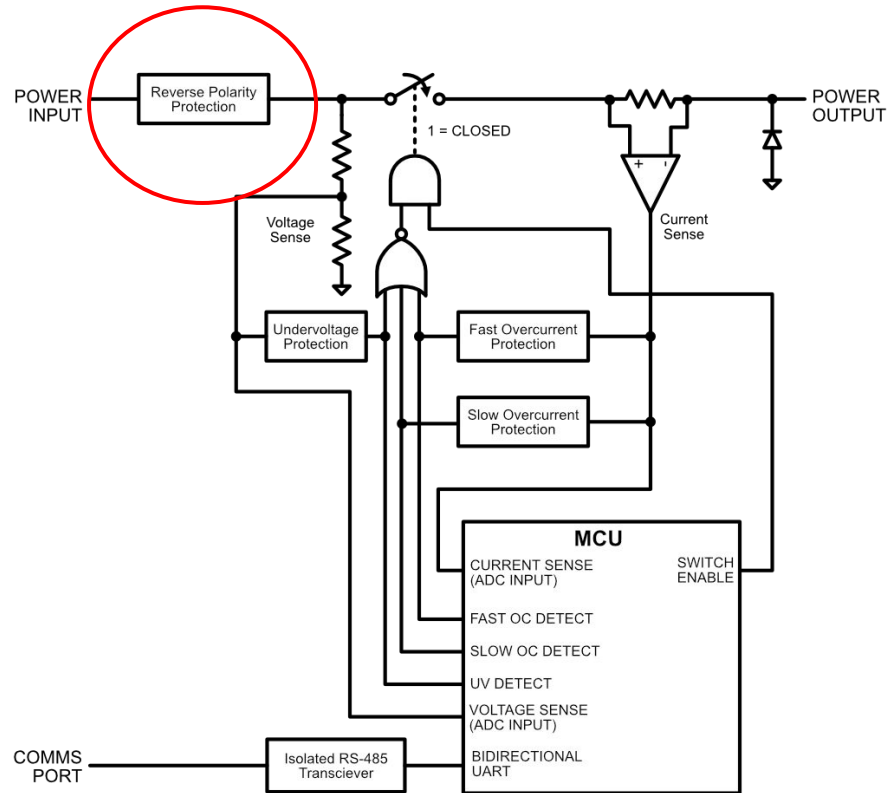


# Power Input

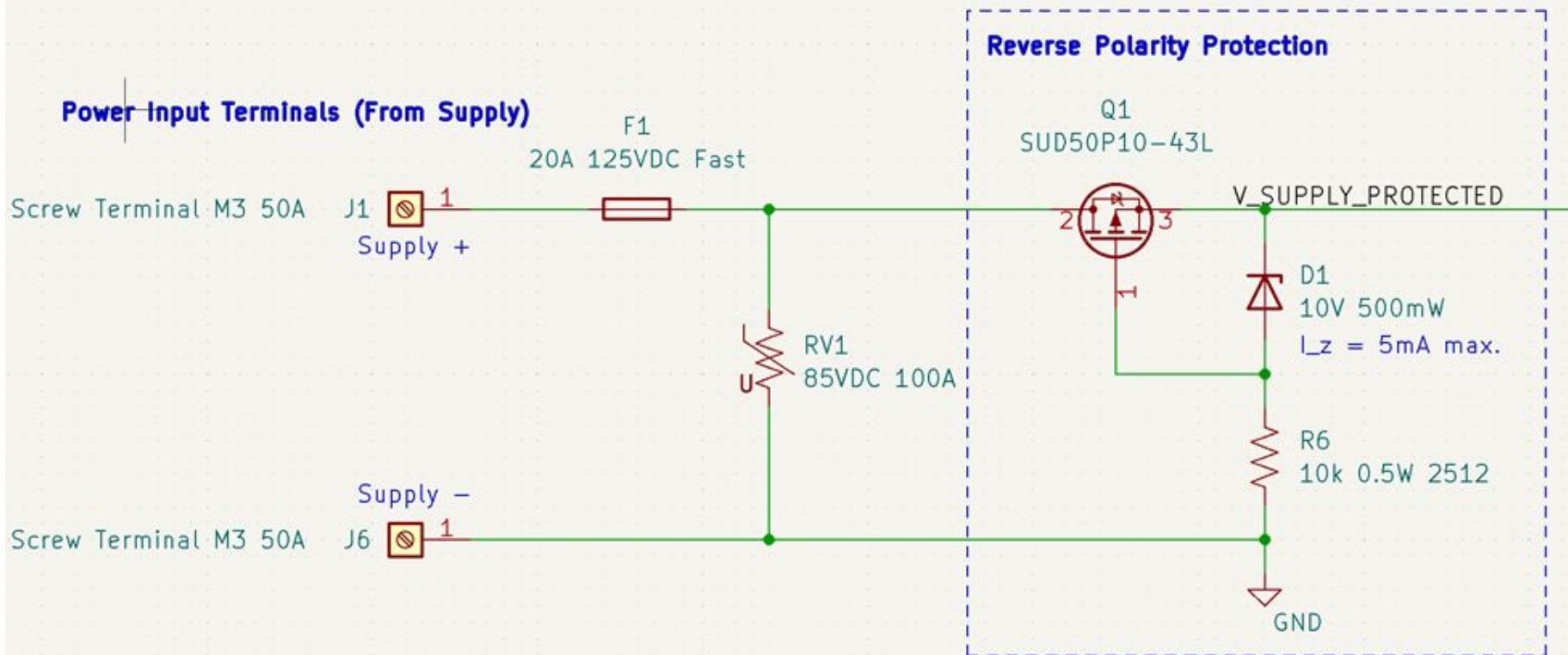





# Simplified Block Diagram: Load Switch

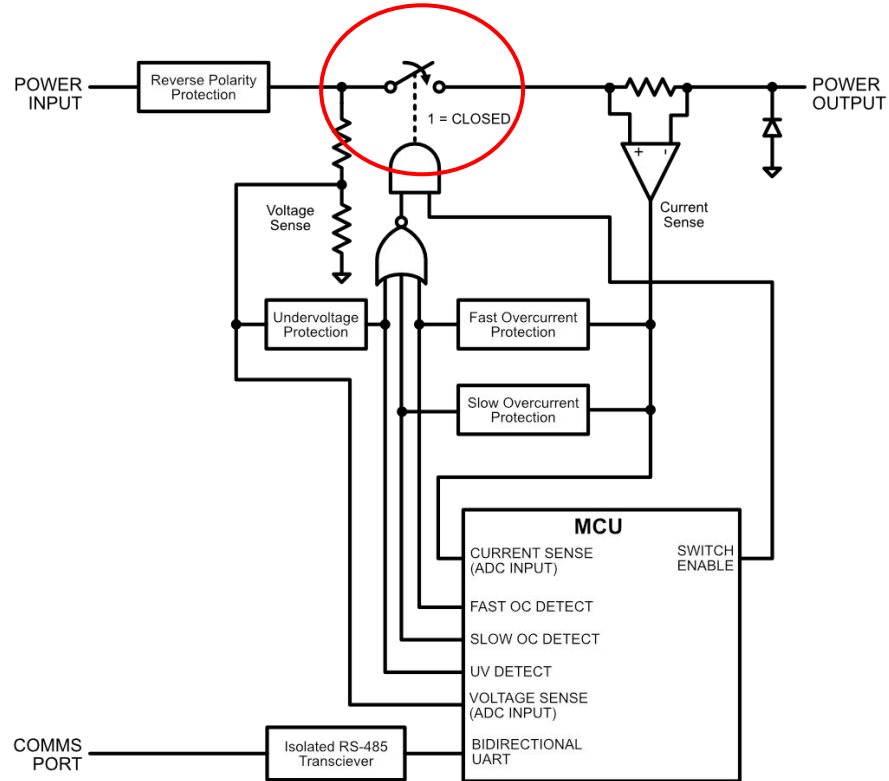


# Load Switch

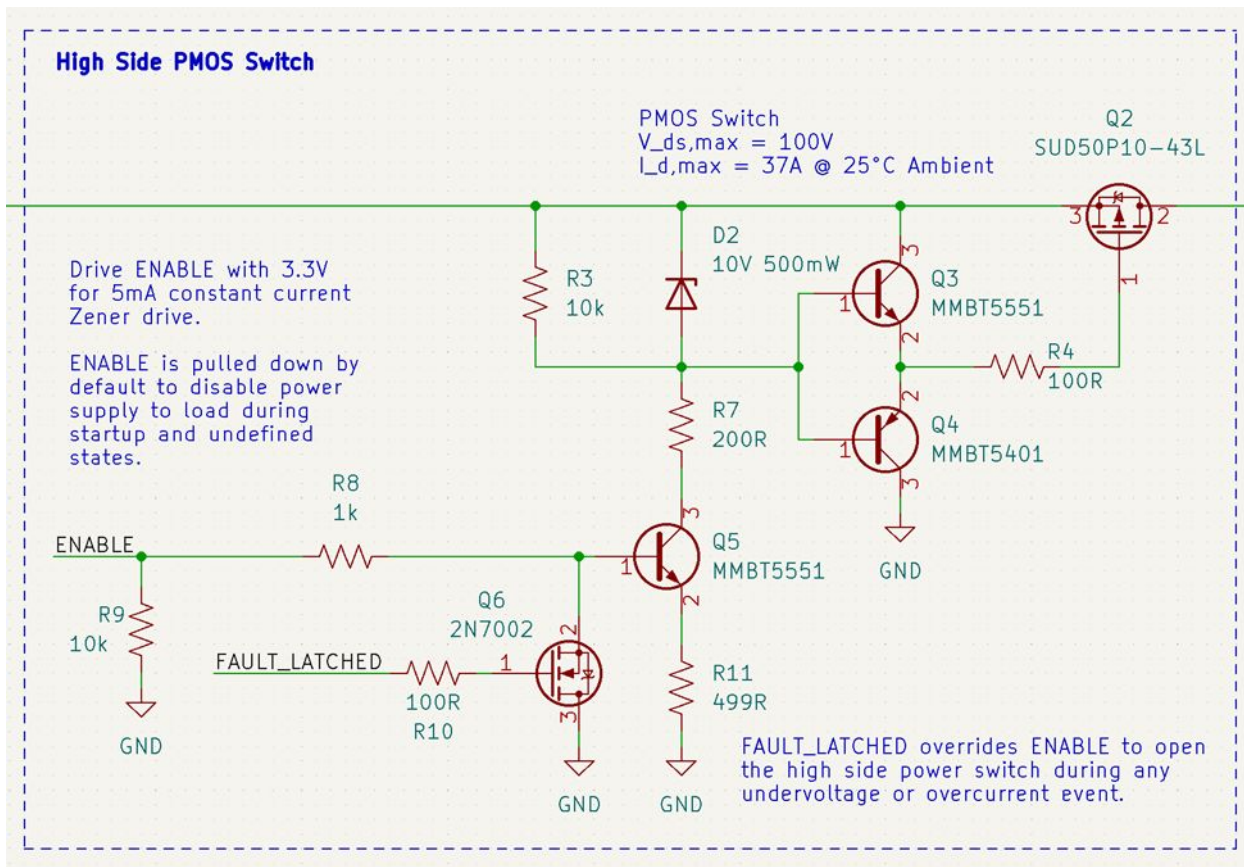

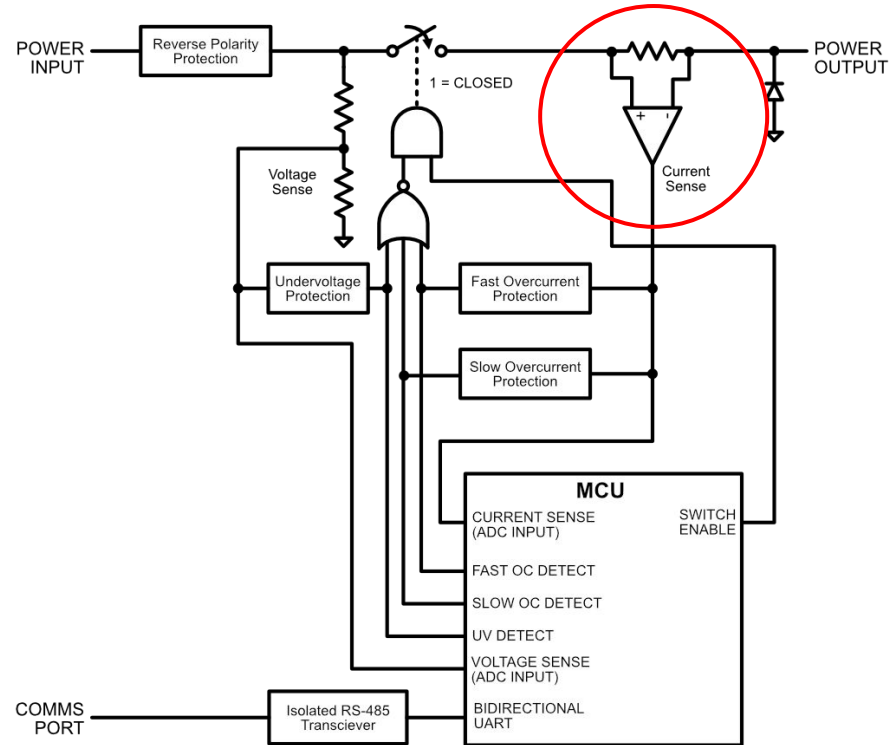
# Simplified Block Diagram: Current Sense






# Current Sense

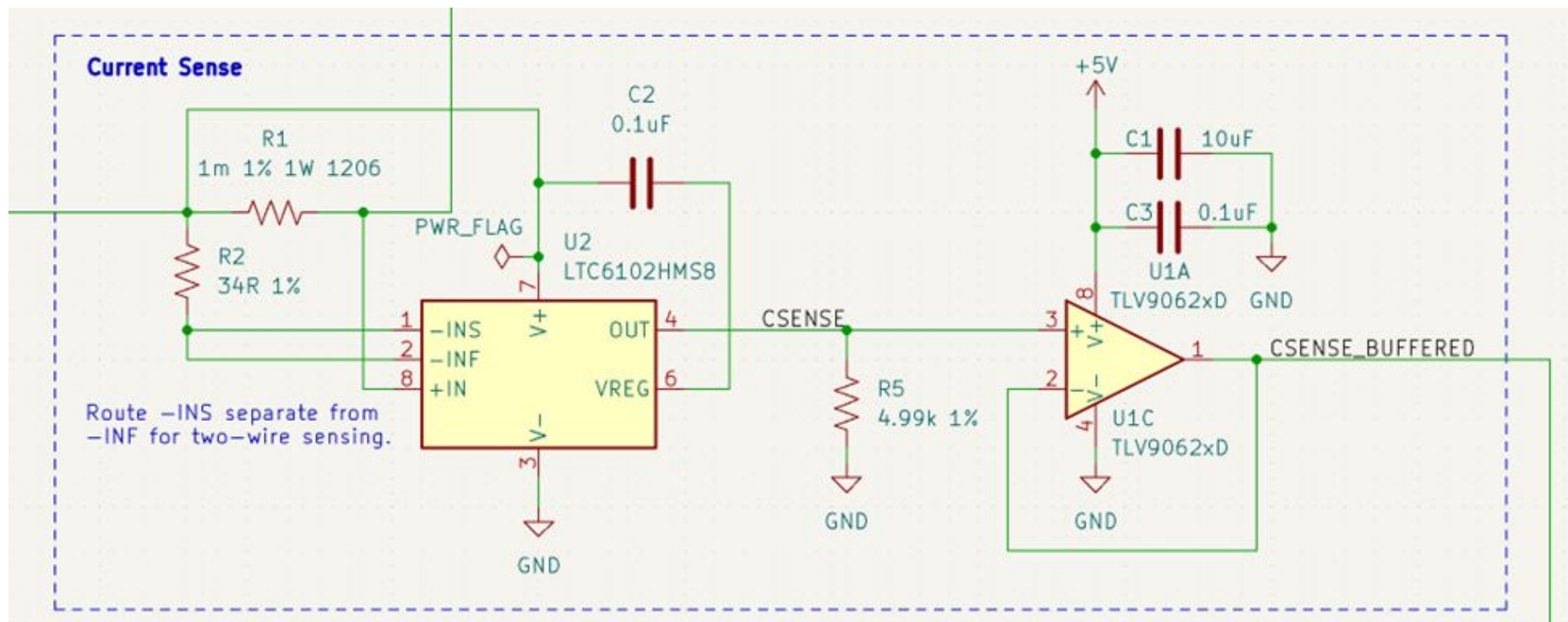

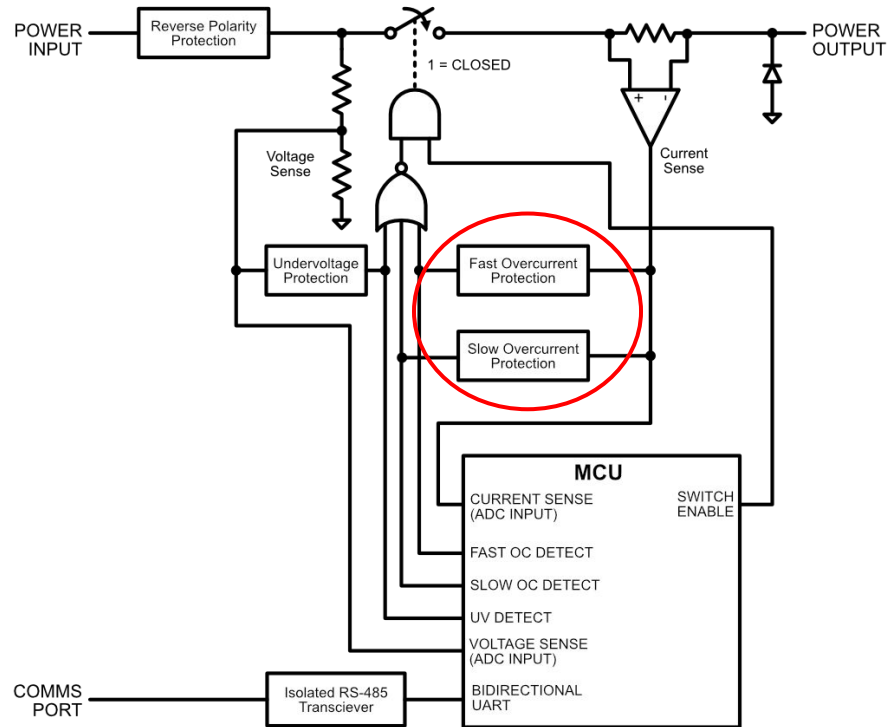
# Simplified Block Diagram: Overcurrent Detection




# Overcurrent Detection

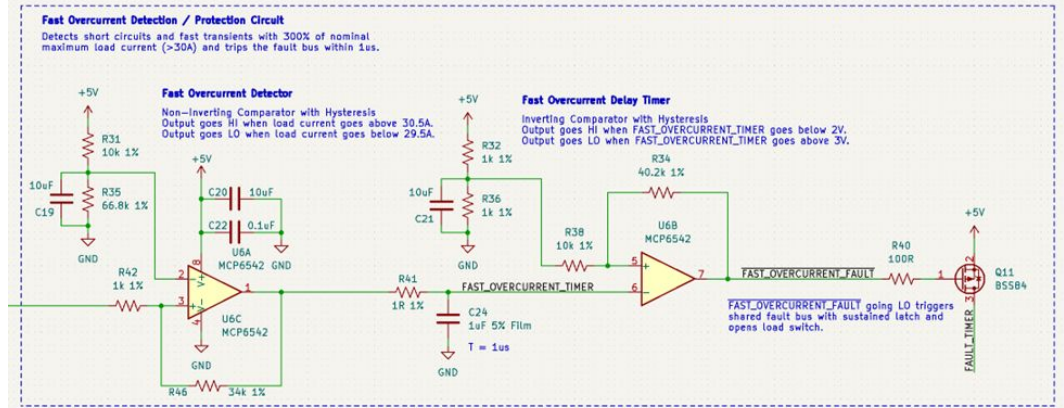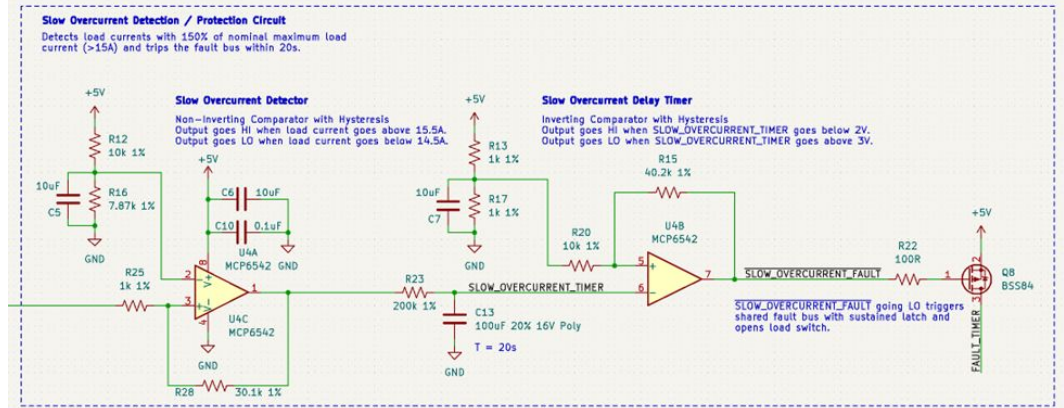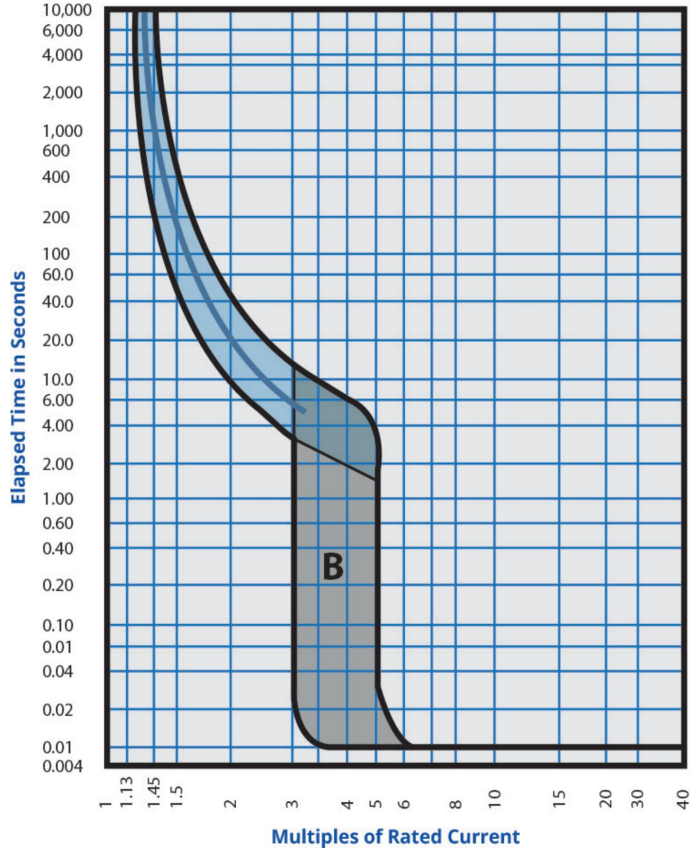

# Overcurrent Detection: PCB Layout

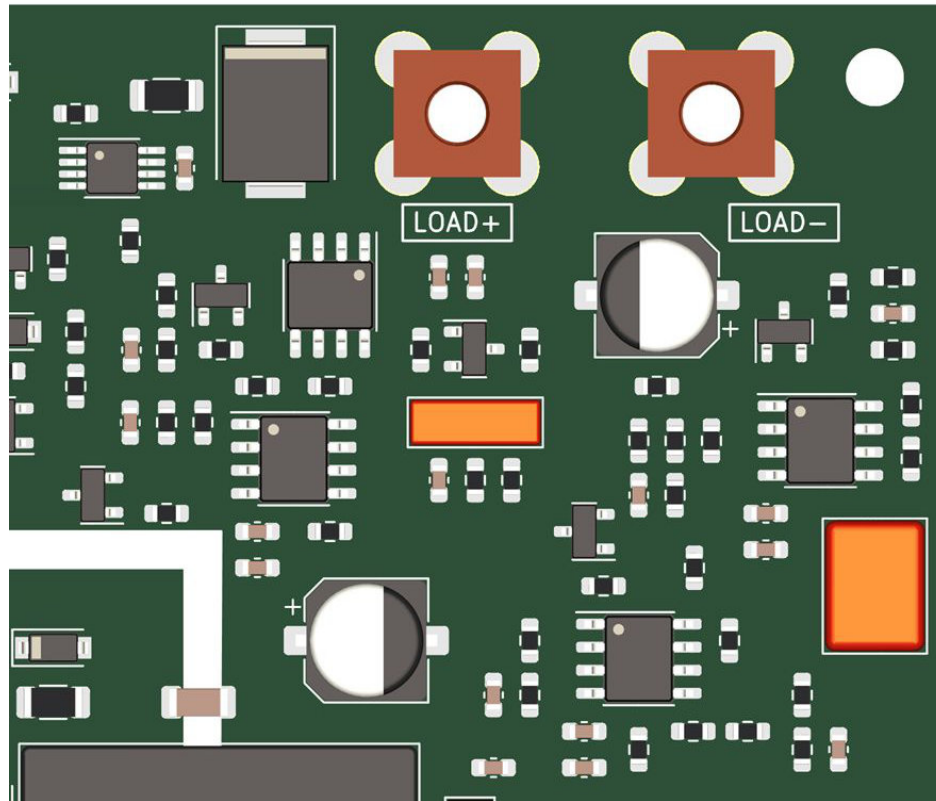

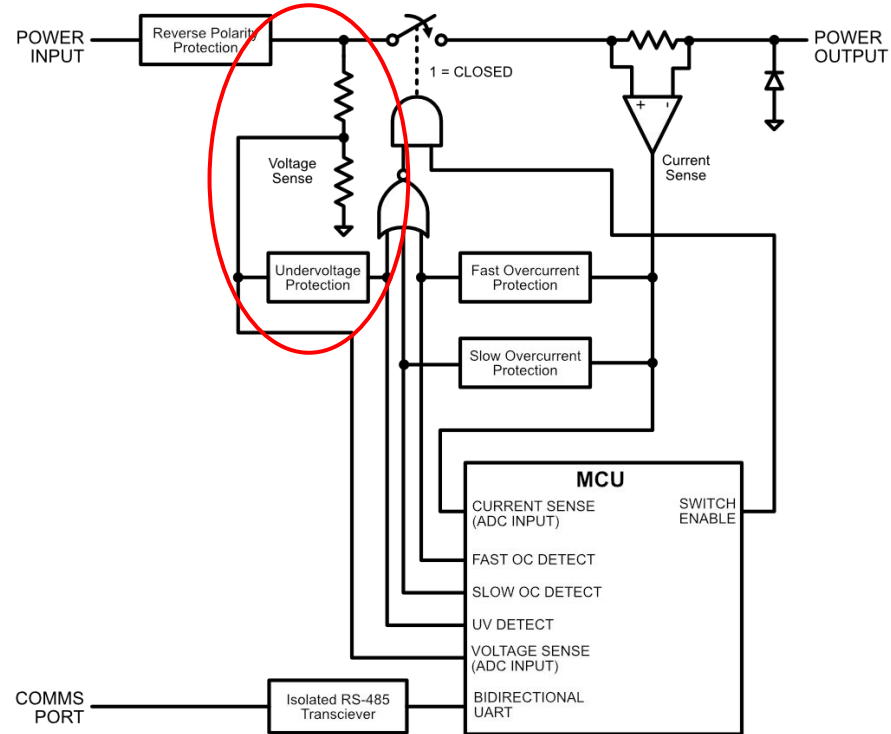
# Simplified Block Diagram: Voltage Sense / UVLO





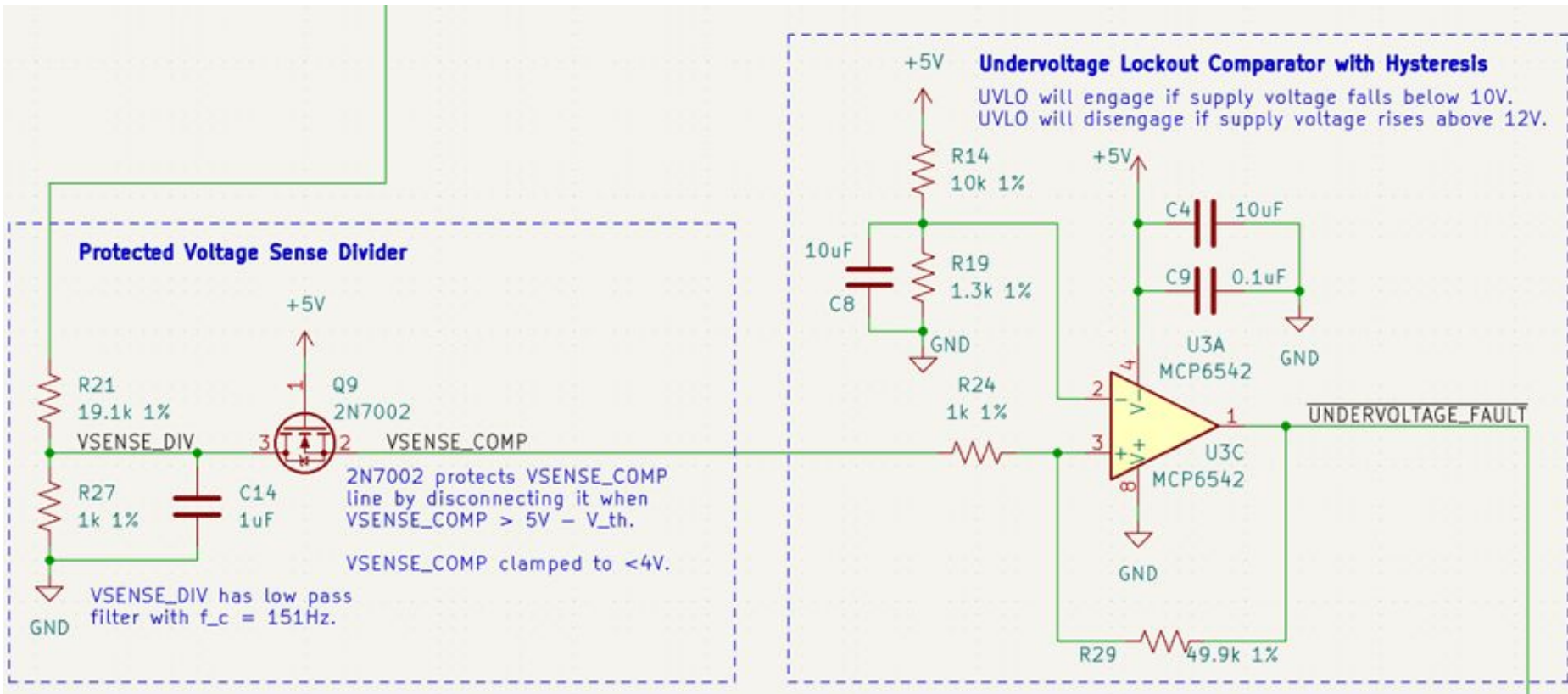
# Voltage Sensing and Undervoltage Detection



# Simplified Block Diagram: Fault Bus

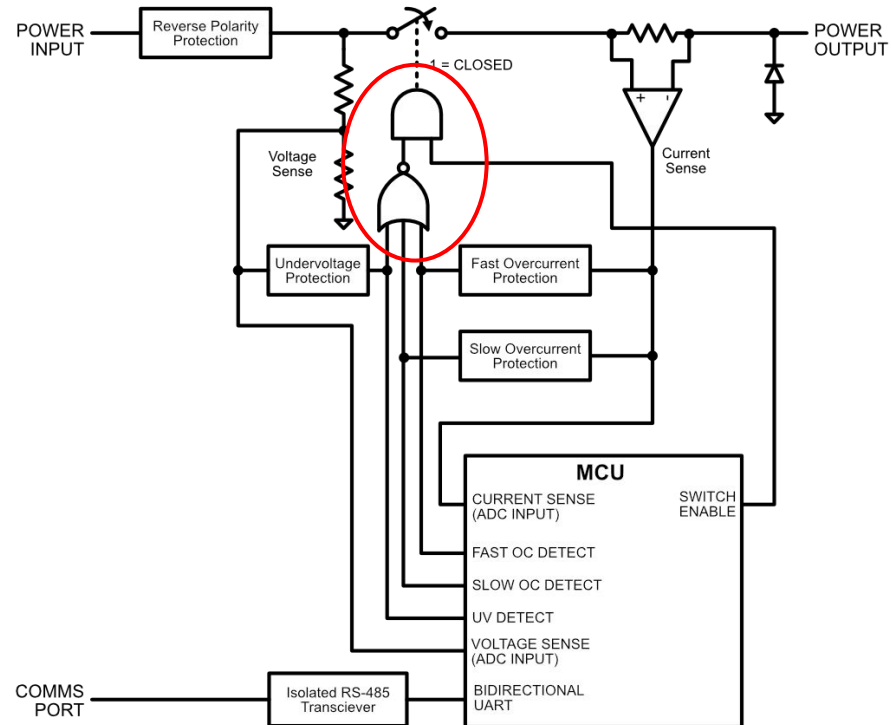


# Shared Fault Bus with Sustained Latch

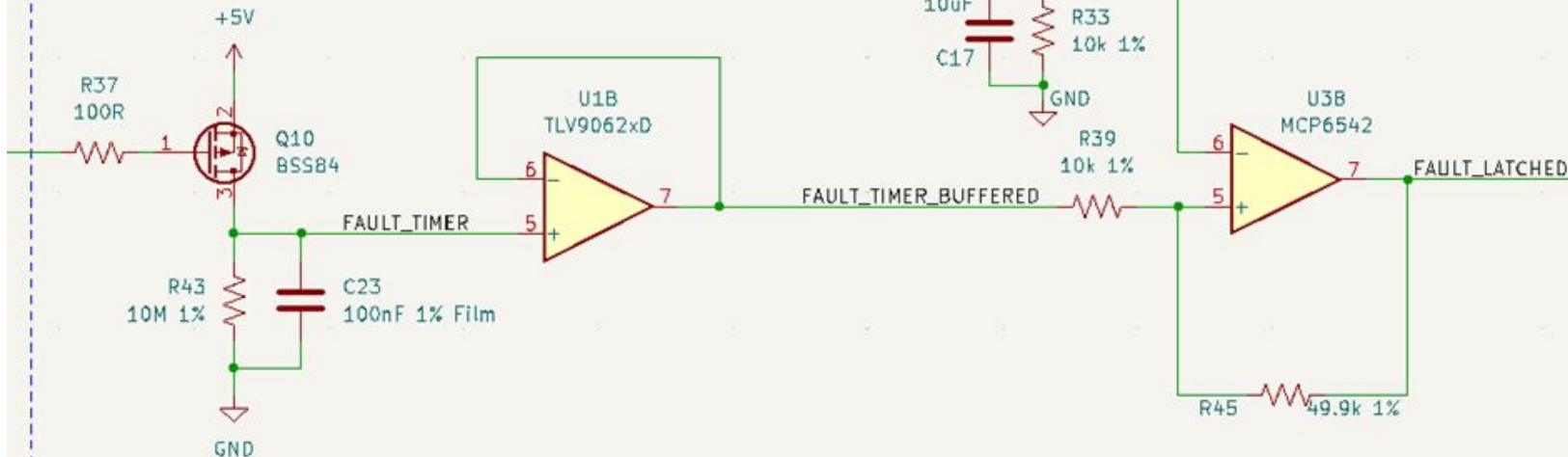
## Shared Fault Bus with Sustained Latch

FAULT\_TIMER bus is shared with undervoltage lockout, fast overcurrent, and slow overcurrent protection comparator circuits.

FAULT\_TIMER charges to 5V when any protection circuit is activated, and slowly discharges with RC time constant of ~1s. FAULT\_LATCHED comparator triggers on FAULT\_TIMER\_BUFFERED output with +/-0.5V hysteresis centered about 2.5V.


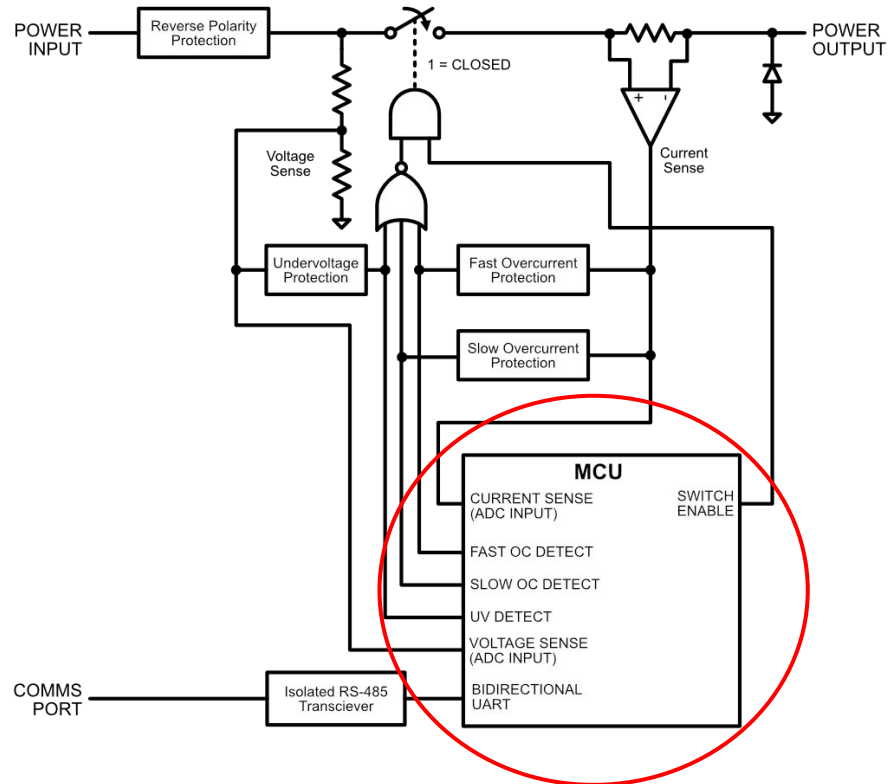
# Simplified Block Diagram: Microcontroller




# Microcontroller

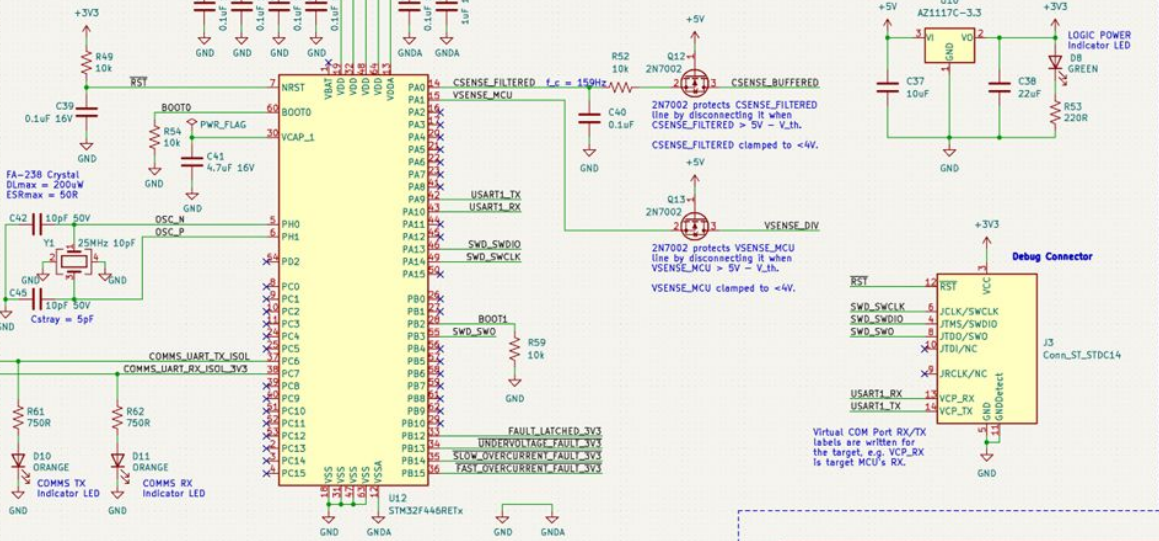
## Microcontroller

Microcontroller provides telemetry and remote control of ENABLE function only. All protection features (undervoltage, overcurrent fast/slow) function independently and can work regardless of microcontroller state.


To boot System Memory, hold BOOT0 high and strobe RST  
To boot User Flash, release BOOT0 and strobe RST



## 5V to 3V3 Level Shifter

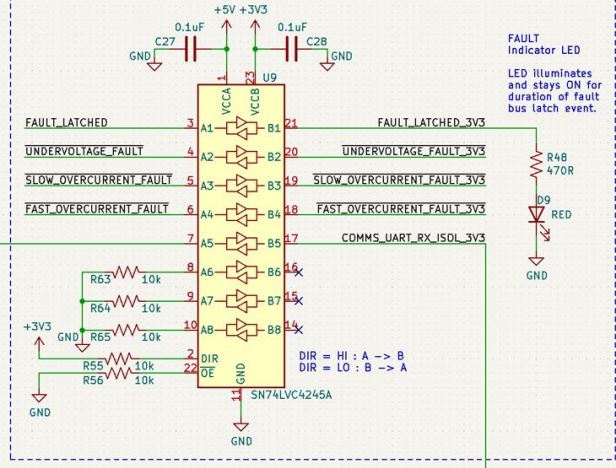

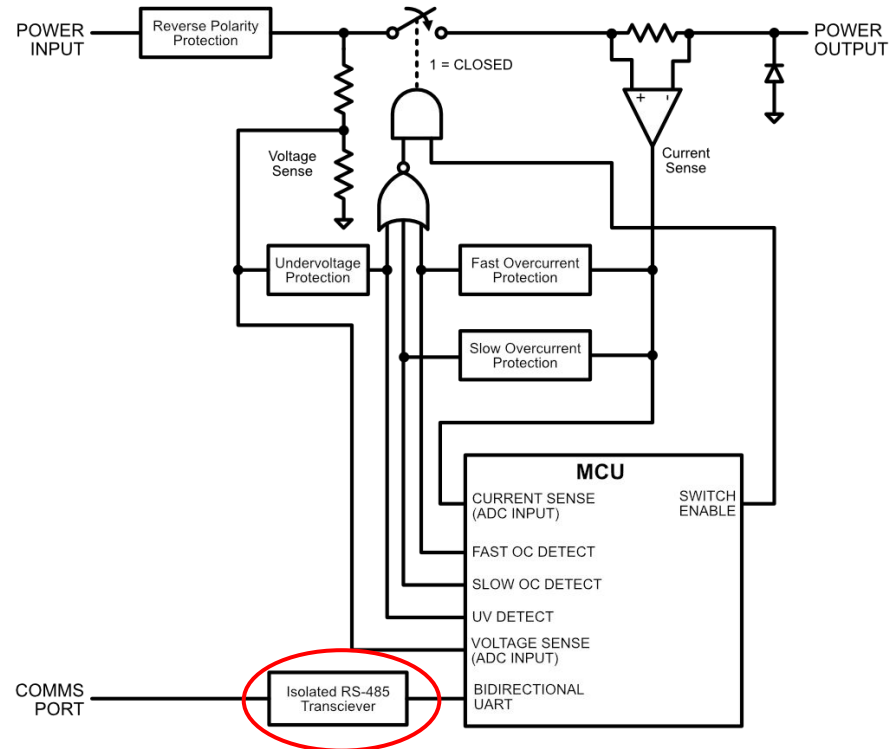
# Simplified Block Diagram: RS-485 Transceiver






# Isolated RS-485 Comms Interface

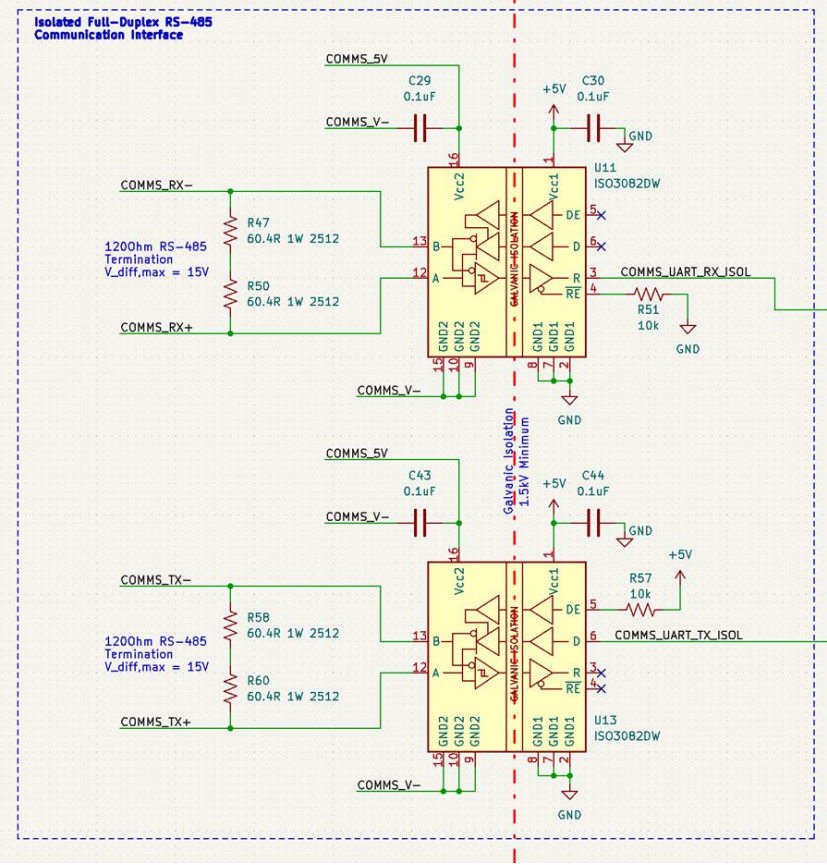
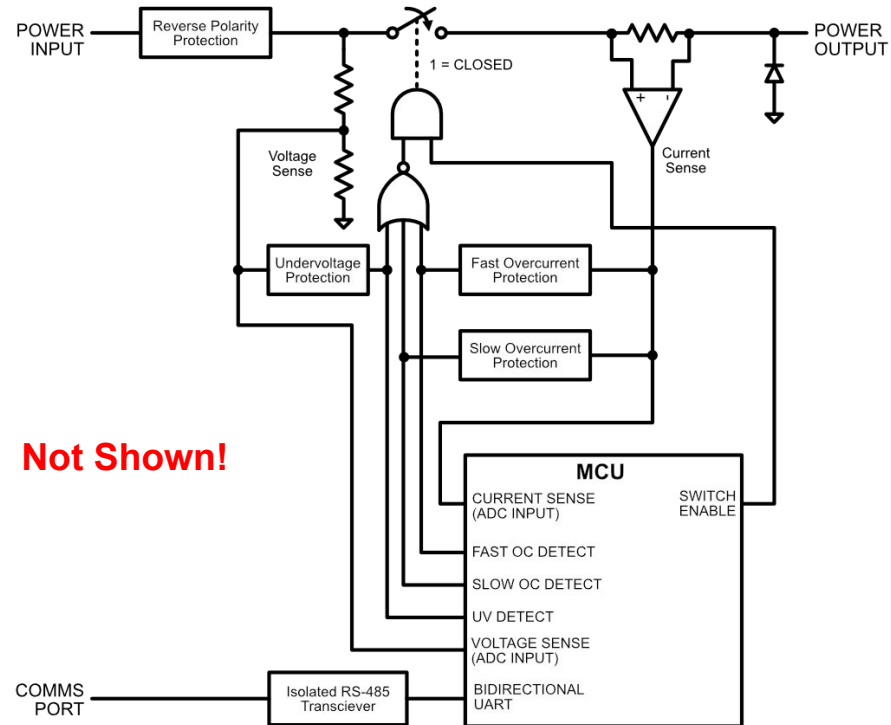
# Simplified Block Diagram: Power Supplies




**Not Shown!**




# Power Supply Protection and Filtering



## Communications Power Conditioning

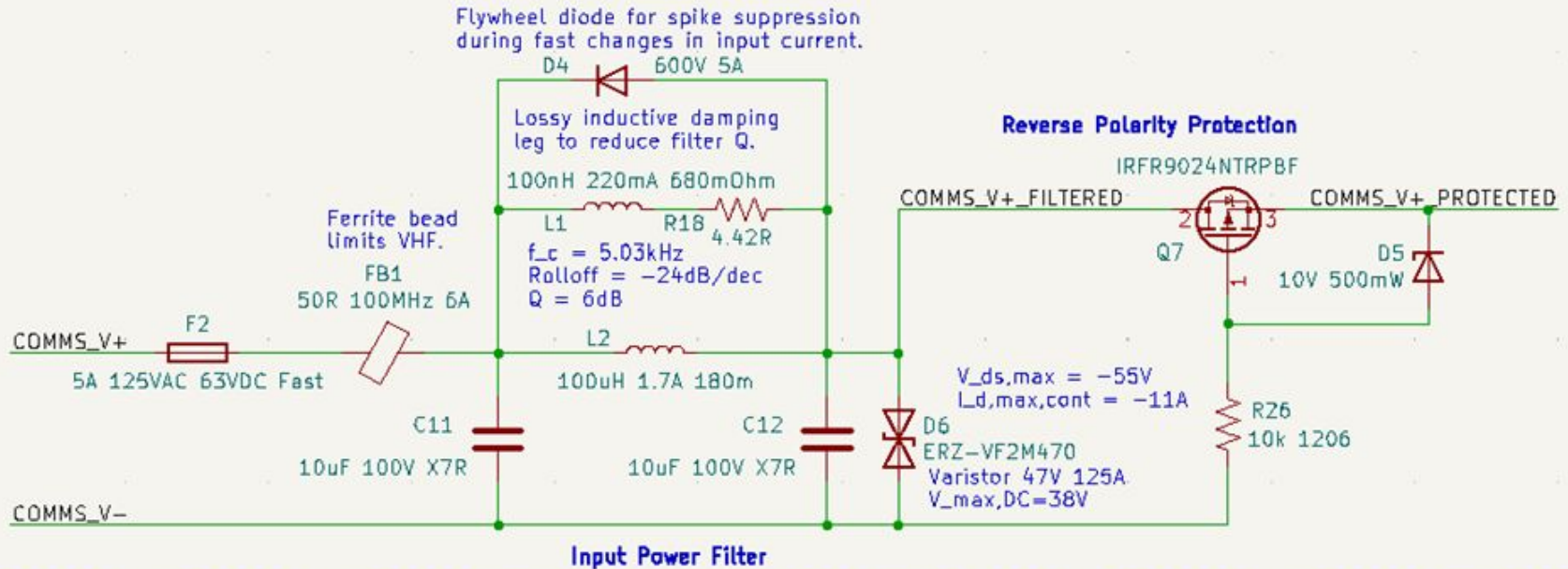

# Power Supplies

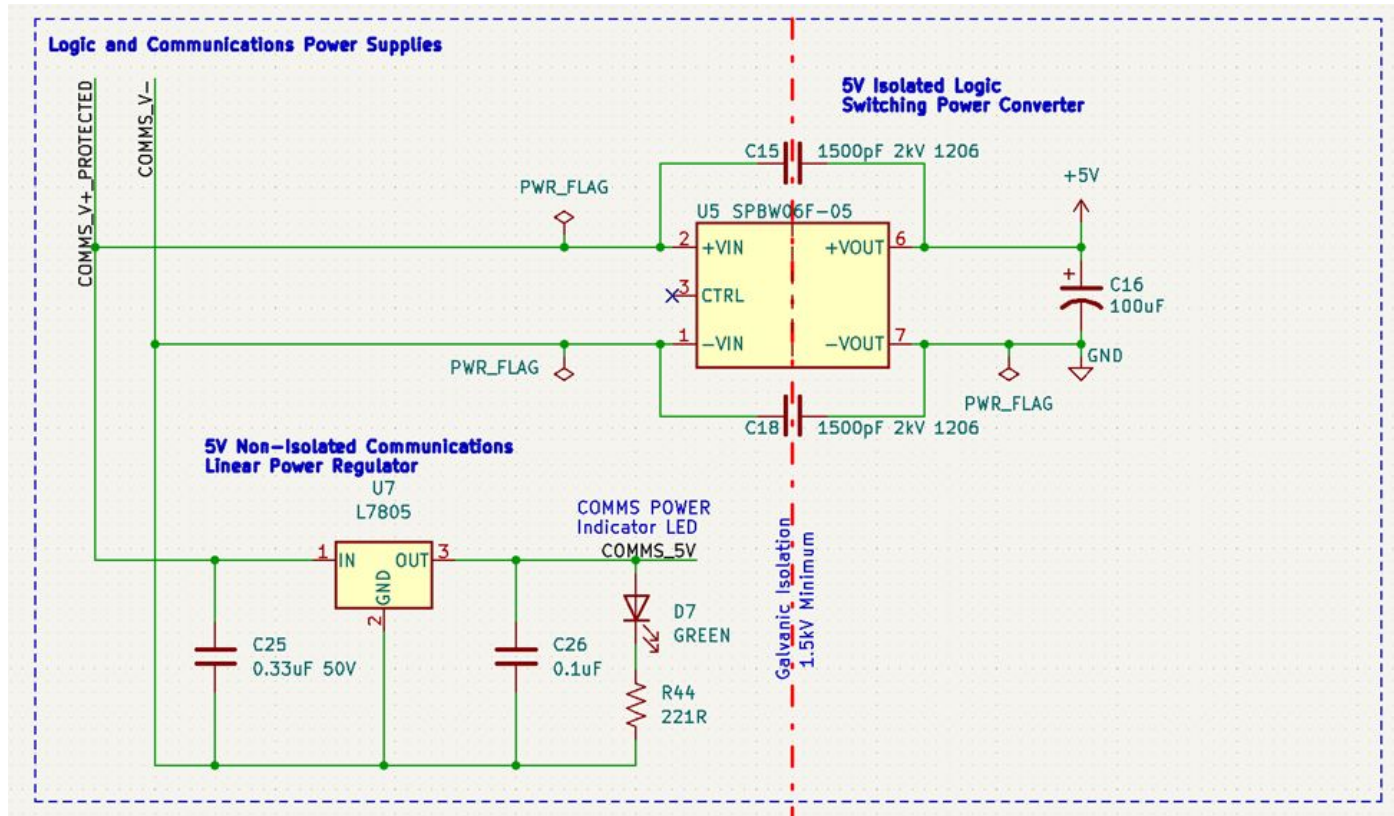

# PCB Layout

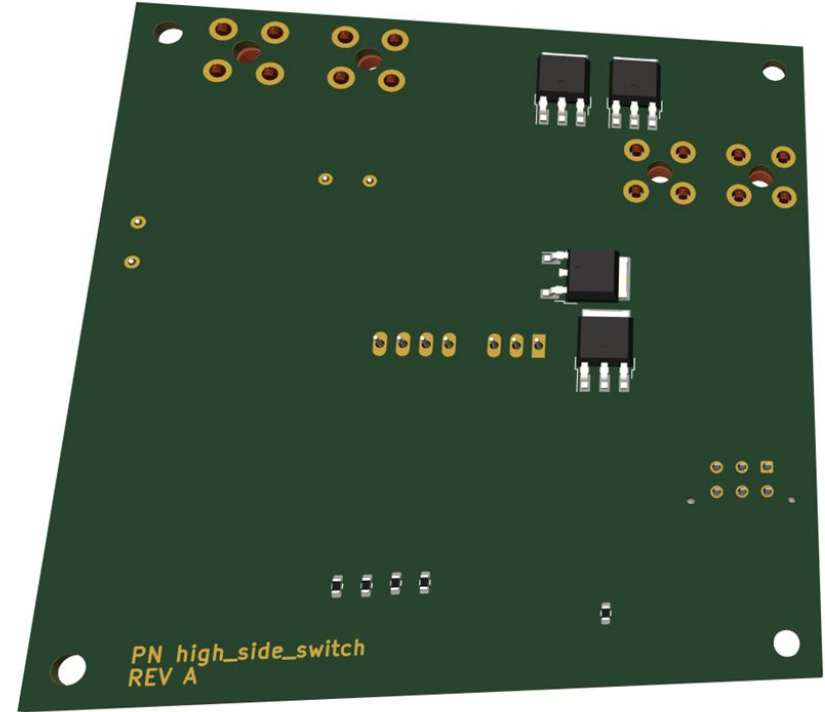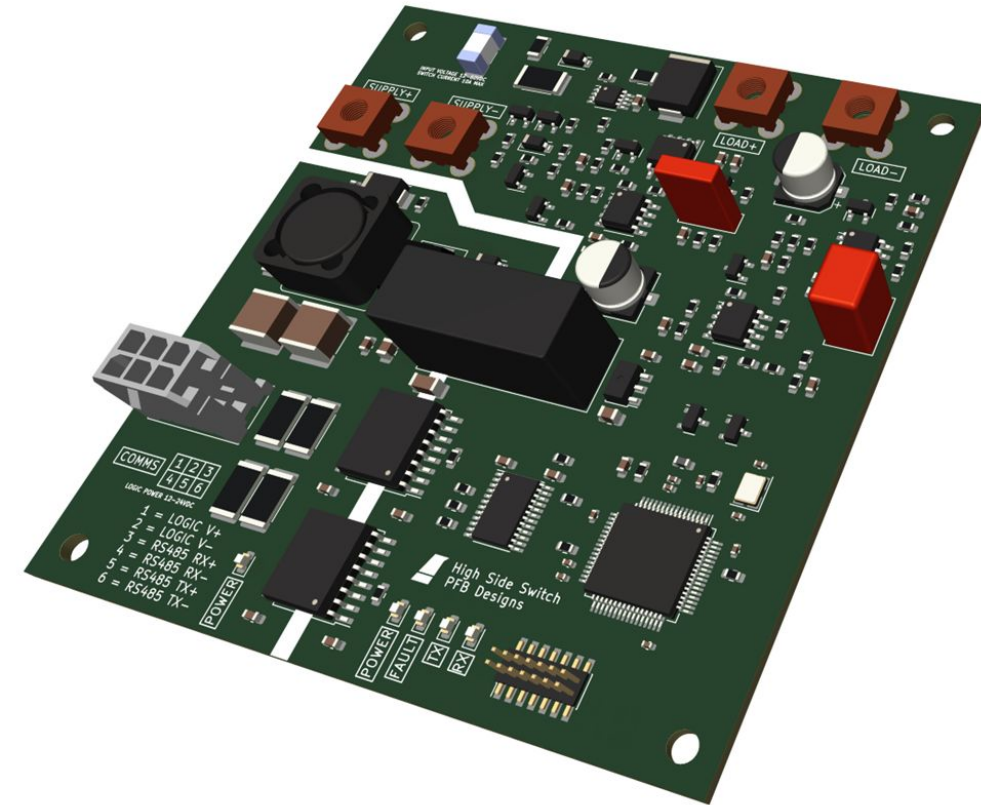

# Backup Slides

Beep beep beep



# Project Links

Project Github: <https://github.com/CoolNamesAllTaken/high-side-switch>